


Chapter 24: Capacitors

Section 24-1: Capacitors

- A capacitor is:

Two conductors with equal and opposite charges

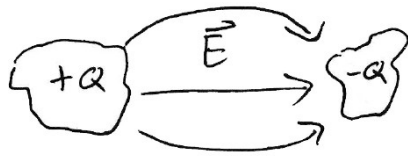Not connected by a conductor (vacuum/insulator between)



- Electric field between them

E is proportional to Q

V is proportional to E

- So Q proportional to V : $Q = CV$


- C is called the capacitance

Constant of proportionality between Q and V

Depends on conductor shape, distance, and material between

- Units are Farads: $F = C/V$

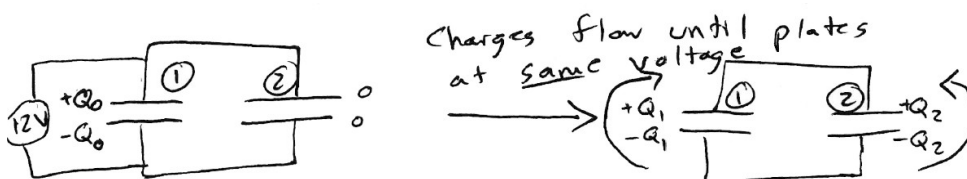Example: A 100 nF capacitor is charged to 12V and disconnected from the battery. It is then connected to an (uncharged) 50 nF capacitor. What is the new voltage on each capacitor?



$$\begin{aligned}
 Q_0 &= C_1 V \\
 &= 100 \times 10^{-9} \text{ F} \cdot 12 \text{ V} \\
 &= 1.2 \times 10^{-6} \text{ C}
 \end{aligned}$$

Same voltage (but opposite directions around loop)

$$Q_1 = C_1 V$$

$$Q_2 = C_2 V$$

$$Q_1 + Q_2 = Q_0$$

$$C_1 V + C_2 V = Q_0$$

$$V = \frac{Q_0}{C_1 + C_2} = \frac{1.2 \times 10^{-6} \text{ C}}{100 \times 10^{-9} \text{ F} + 50 \times 10^{-9} \text{ F}} = \boxed{8 \text{ V}}$$

Section 24-2: Determination of Capacitance


- Most capacitors are parallel plates
- If size of plates larger than distance between, use infinite plane

$$E = \frac{\sigma}{2\epsilon_0} \text{ (per plate)}$$

$$E = -\frac{\sigma}{\epsilon_0} \text{ (two plates, left)}$$


$$V = -E\Delta x = -\left(-\frac{\sigma}{\epsilon_0}\right)d = \frac{Qd}{A\epsilon_0}$$


$$C = \frac{Q}{V} = \frac{Q}{\left(\frac{Qd}{A\epsilon_0}\right)} \quad \text{so} \quad \boxed{C = \frac{A\epsilon_0}{d}}$$

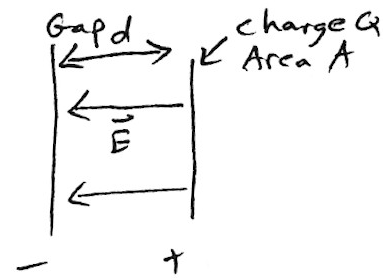

Section 24-3: Series and Parallel Capacitors

- Circuit diagram symbols:

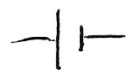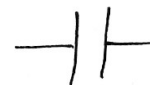 Voltage source
(Battery or power supply)


 Capacitor

- Parallel:

Choice: one or other never both

Voltage V the same

Charges add $Q = Q_1 + Q_2$

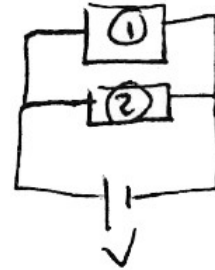


- Series:

No choices: every charge through both

Charge Q the same

$V = V_1 + V_2$ since energy changes add

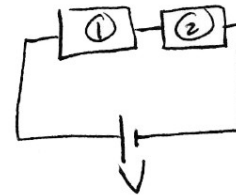


- Parallel Capacitors:

Same voltage V (no subscript)

$$Q_1 = C_1 V \text{ and } Q_2 = C_2 V$$

$$Q = Q_1 + Q_2 = C_1 V + C_2 V = (C_1 + C_2) V$$

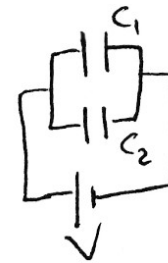Acts like one capacitor with $C_{par} = C_1 + C_2$



Three capacitors: $C_{par} = C_1 + C_2 + C_3$, etc.


- Series Capacitors:

Same charge Q (no subscript)


$$V_1 = \frac{Q}{C_1} \text{ and } V_2 = \frac{Q}{C_2}$$

$$V = V_1 + V_2 = \frac{Q}{C_1} + \frac{Q}{C_2} = \left(\frac{1}{C_1} + \frac{1}{C_2} \right) Q$$
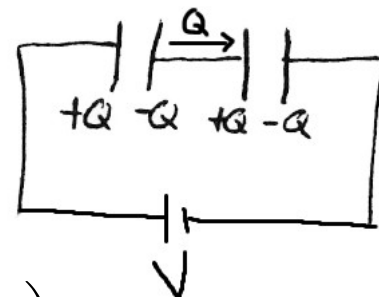
$$Q = \left(\frac{1}{C_1} + \frac{1}{C_2} \right)^{-1} V$$






Book / HW draw as:

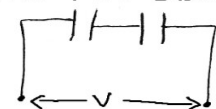

Acts like single capacitor with $\boxed{\frac{1}{C_{ser}} = \frac{1}{C_1} + \frac{1}{C_2}}$

C_{ser} necessarily smaller than both C_1 and C_2

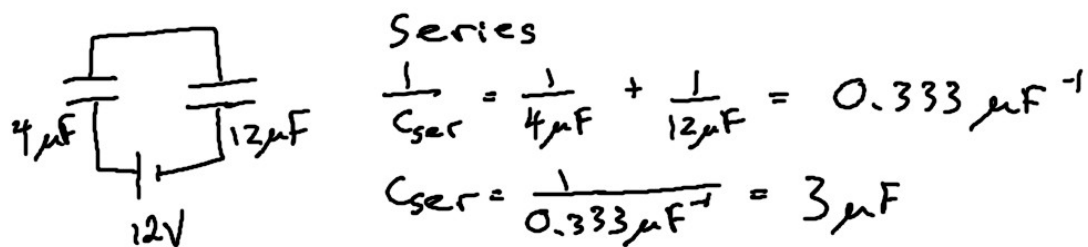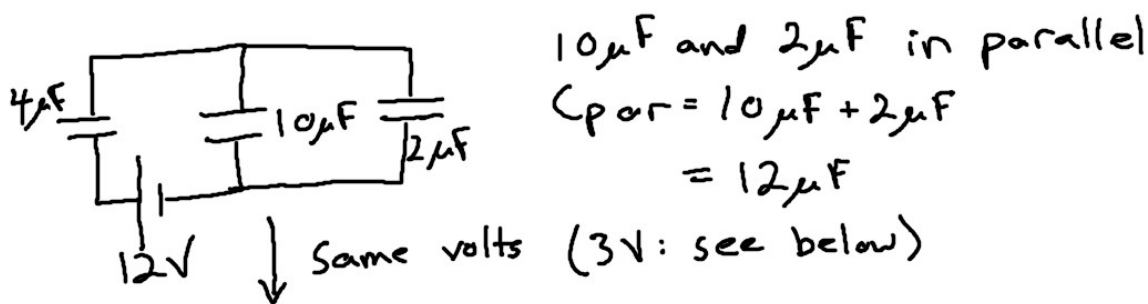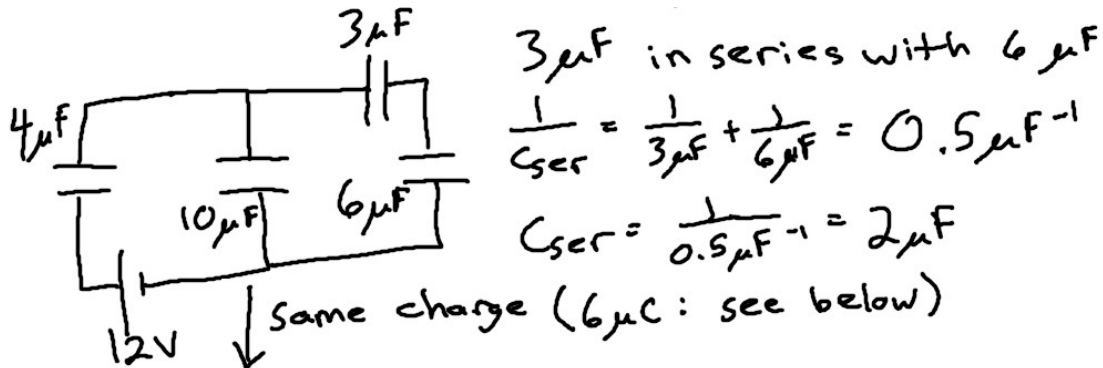Example: Find the voltage on the $3\mu F$ capacitor.



$$Q = CV = 3\mu F \cdot 12V = 36\mu C$$

Voltage on $12\mu F$ in last diagram:

$$V = \frac{Q}{C} = \frac{36\mu C}{12\mu F} = 3V \text{ (same volts in middle diagram)}$$


Charge on $2\mu F$ in middle diagram:

$$Q = CV = 2\mu F \cdot 3V = 6\mu C \text{ (same charge in 1st diagram)}$$

Voltage on $3\mu\text{F}$ in 1st diagram:

$$V = \frac{Q}{C} = \frac{6\mu\text{C}}{3\mu\text{F}} = \boxed{2\text{V}}$$

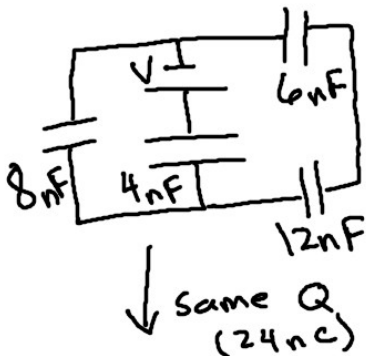Example: If the 6nF has 4V , find the voltage of the battery




Q on 6nF : $Q = CV = 6\text{nF} \cdot 4\text{V} = 24\text{nC}$

6nF in series with 12nF :

$$\frac{1}{C_{\text{ser}}} = \frac{1}{6\text{nF}} + \frac{1}{12\text{nF}} = 0.25\text{nF}^{-1}$$

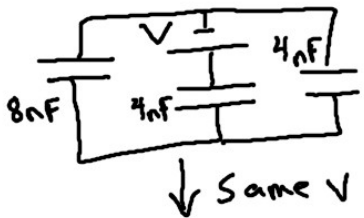
$$C_{\text{ser}} = \frac{1}{0.25\text{nF}^{-1}} = 4\text{nF}$$



V on right-hand 4nF : $V = \frac{Q}{C} = \frac{24\text{nC}}{4\text{nF}} = 6\text{V}$

4nF in parallel with 8nF
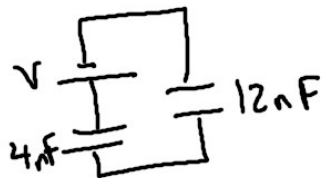
$$C_{\text{par}} = 4\text{nF} + 8\text{nF} = 12\text{nF}$$



Q on 12nF : $Q = CV = 12\text{nF} \cdot 6\text{V} = 72\text{nC}$

Series: $\frac{1}{C_{\text{ser}}} = \frac{1}{4\text{nF}} + \frac{1}{12\text{nF}} = 0.333\text{nF}^{-1}$

$$C_{\text{ser}} = \frac{1}{0.333\text{nF}^{-1}} = 3\text{nF}$$

$$V = \frac{Q}{C} = \frac{72\text{nC}}{3\text{nF}} = \boxed{24\text{V}}$$

Section 24-4: Electric Field Energy

- Charging a capacitor to final charge Q :

Small dQ goes from pos. to neg.

Energy change $dU = VdQ$

- Final energy is U , initially empty so $U_0 = 0$

- Total energy gain:

$$\Delta U = \int dU$$

$$U - U_0 = \int_0^Q V dQ \quad (\text{initial charge } 0, \text{ final is } Q)$$

$$U = \int_0^Q \frac{Q}{C} dQ \quad (\text{using } Q = CV \text{ and also using } U_0 = 0)$$

$$\boxed{U = \frac{1}{2} \frac{Q^2}{C}} \quad (\Delta U = U \text{ since } U_0 = 0)$$

- Plugging in $Q = CV$ gives $\boxed{U = \frac{1}{2} CV^2}$

Example: $1\mu\text{F}$ and $2\mu\text{F}$ capacitor are connected in series to a 15 V supply. What is the energy of the capacitors?

$$\frac{1}{C_{\text{ser}}} = \frac{1}{1\mu\text{F}} + \frac{1}{2\mu\text{F}} = 1.5\mu\text{F}^{-1}$$

$$C_{\text{ser}} = 0.667\mu\text{F}$$

$$U = \frac{1}{2} C_{\text{ser}} V^2 = \frac{1}{2} (0.667 \times 10^{-6} \text{ F}) (15 \text{ V})^2 = \boxed{7.5 \times 10^{-5} \text{ J}}$$


Section 24-5: Dielectrics

- Dielectric materials are the same thing as insulators

When discussing conduction of electricity: insulator

When discussing capacitors: dielectric

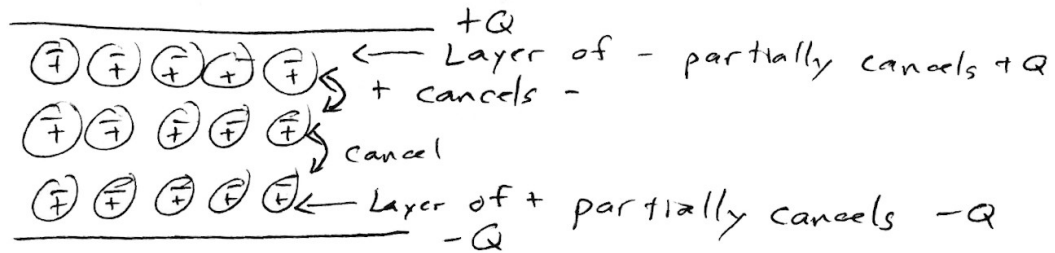- For a given amount of charge, will reduce voltage



- Replace ϵ_0 by ϵ in formulas

Vacuum: $C_{vac} = \frac{A\epsilon_0}{d}$

Dielectric: $C = \frac{A\epsilon}{d}$

ϵ (permittivity of some material) larger than ϵ_0

- Dielectric constant K :

$$K = \frac{\epsilon}{\epsilon_0}$$


$$\boxed{C = KC_{vac}}$$

- Since $\epsilon > \epsilon_0$, $K > 1$
- Use table in book, not values you find online (given on exams)


Table on page 703 (print edition), Section 24-5

- Scaling:

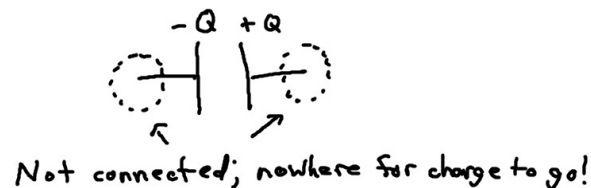Not connected to battery: Q must stay constant



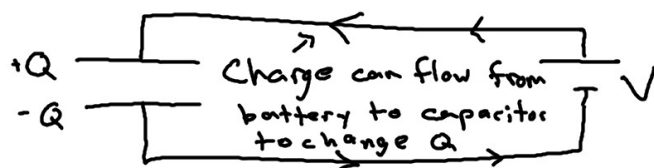Connected to battery: battery maintains constant V



Batteries raise voltage of connected device to battery's voltage

Example: A capacitor is charged up to 12V and disconnected from the battery. A $K=3$ material is then inserted. What is the new voltage?

If disconnected from battery, $Q = \text{constant}$

$$Q = C V \leftarrow V \text{ must be multiplied by } \frac{1}{3} \text{ since } Q \text{ must stay the same while } C \text{ triples}$$

\uparrow \uparrow
 same times 3

$$12V \times \frac{1}{3} = \boxed{4V}$$

Example: An air filled capacitor is made of square plates 10cm on a side and 2mm apart. It is charged up to 15V and kept connected to the battery. What is the change in energy if it is then filled with a $K=4$ material?

$$C = \frac{\epsilon_0 A}{d} = \frac{8.85 \times 10^{-12} \text{ Nm}^2/\text{C}^2 \cdot (0.1\text{m})^2}{0.002\text{m}} = 4.425 \times 10^{-11} \text{ F}$$

$$U_0 = \frac{1}{2} C V^2 = \frac{1}{2} \cdot 4.425 \times 10^{-11} \text{ F} \cdot (15\text{V})^2 = 4.98 \times 10^{-9} \text{ J}$$

$$U = \frac{1}{2} C V^2 \leftarrow \text{Constant so } U = 4U_0 = 4 \cdot 4.98 \times 10^{-9} \text{ J} = 1.99 \times 10^{-8} \text{ J}$$

\uparrow \uparrow \uparrow
 Must be 4 times 4 times

$$\Delta U = U - U_0 = 1.99 \times 10^{-8} \text{ J} - 4.98 \times 10^{-9} \text{ J} = \boxed{1.49 \times 10^{-8} \text{ J}}$$

Example: While connected to a battery, the distance between plates of a capacitor is doubled. What happens to (a) the charge, (b) the energy?

$$C = \frac{A\epsilon_0}{d} \quad \text{Double } d \Rightarrow C \text{ cut in half.}$$

Connected to battery: $V = \text{const}$

(a) $Q = CV$

C is $\frac{1}{2}$, $V = \text{const}$, so $Q = \boxed{\frac{1}{2}}$

(b) $U = \frac{1}{2} CV^2$ $U = \frac{1}{2} \frac{Q^2}{C}$

↑
Easier
($V = \text{const}$)

↑
Harder to analyze (both Q and C change)

C is half, so U cut in $\boxed{\text{half}}$

Homework: Do Chapter 24 in Mastering Physics