


Chapter 26: DC Circuits

Section 26-1: EMF

- Batteries have resistance called internal resistance r
- Resistance decreases voltage by Ir (Ohm's Law)
- Terminal voltage is actual voltage of battery, including resistance
- Electromotive force (emf) is voltage when no current flows

$$\boxed{V = \mathcal{E} - Ir}$$

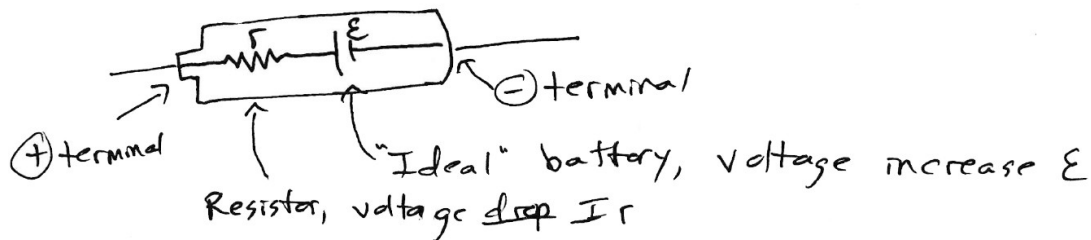- A real battery can be thought of as a series circuit:



- Overall voltage across both is $\mathcal{E} - Ir$


Section 26-2: Series and Parallel Resistors

- Recall rules of circuits:

- Series:

Voltages add, $V = V_1 + V_2$


Same charge Q , so same current I

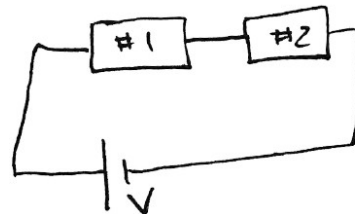

- Parallel:

Same voltage V

Currents add, $I = I_1 + I_2$

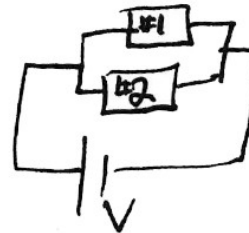

- Series resistors

$$V = V_1 + V_2 = IR_1 + IR_2 = I(R_1 + R_2)$$

So series circuit acts like single resistor $R_{ser} = R_1 + R_2$

Note this is the same as parallel capacitors

N identical resistors: $R_{ser} = R + R + R + \dots$ or $R_{ser} = NR$

More in series gives bigger resistance

- Parallel resistors

$$I = I_1 + I_2$$

$$\frac{V}{R_{par}} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$\frac{1}{R_{par}} = \frac{1}{R_1} + \frac{1}{R_2}$$

Note this is the same as series capacitors

N identical in parallel: $\frac{1}{R_{par}} = \frac{1}{R} + \frac{1}{R} + \dots = \frac{N}{R}$ or $R_{par} = \frac{R}{N}$

More resistors in parallel makes resistance smaller

Example: A 1.5V battery has 0.05 Ω internal resistance.
How much power will it deliver to a 5 Ω light bulb?



Treat real battery
as ideal battery
and resistor in series

$$R_{ser} = 5 \Omega + 0.05 \Omega = 5.05 \Omega$$

$$V = IR_{ser} \text{ so } I = \frac{V}{R_{ser}} = \frac{1.5V}{5.05 \Omega} = 0.297 A$$


Don't use $P = VI$ or $P = \frac{V^2}{R}$ since we don't know V for light bulb

$$P = I^2 R = (0.297 A)^2 \cdot 5 \Omega = 0.441 W$$

Resistance of bulb to find bulb's power

[May skip this example if time is short.]

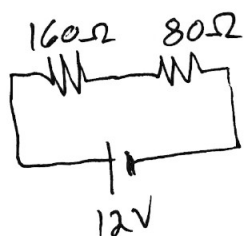Example: A 12 V battery is connected in series to a $160\ \Omega$ and an $80\ \Omega$ resistor. What is the voltage drop on the $80\ \Omega$ resistor?




Whole circuit: $R_{eq} = 160\ \Omega + 80\ \Omega = 240\ \Omega$

$$V = I R_{eq}$$

$$I = \frac{V}{R_{eq}} = \frac{12\text{V}}{240\ \Omega} = 0.05\text{ A}$$



$80\ \Omega$ resistor: $V = I R = 0.05\text{ A} \cdot 80\ \Omega$
 $= \boxed{4\text{ V}}$

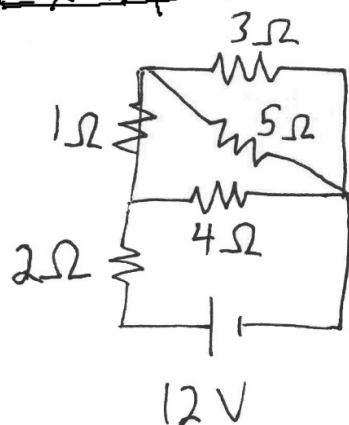Example: Find the current in the $3\ \Omega$ resistor




$$\frac{1}{R_{par}} = \frac{1}{3\ \Omega} + \frac{1}{5\ \Omega} = 0.533\ \Omega^{-1}$$

$$R_{par} = 1.88\ \Omega$$

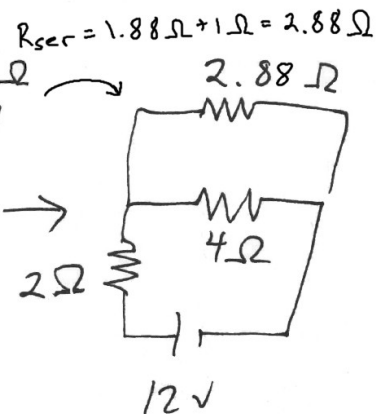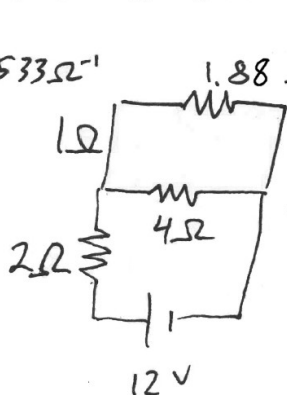

$$\frac{1}{R_{par}} = \frac{1}{2.88\ \Omega} + \frac{1}{4\ \Omega} = 0.598\ \Omega^{-1}$$

$$R_{par} = 1.67\ \Omega$$

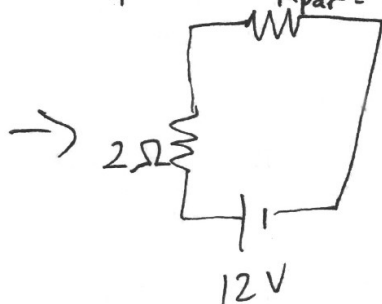

$$R_{ser} = 2\ \Omega + 1.67\ \Omega = 3.67\ \Omega$$

Total resistance: $3.67\ \Omega$

$$I = \frac{V}{R} = \frac{12\text{ V}}{3.67\ \Omega} = 3.27\text{ A}$$

Voltage on 1.67Ω (last diagram):

$$V = IR = 3.27\text{ A} \cdot 1.67\Omega = 5.46\text{ V} \quad \rightarrow \text{Parallel: Same } V$$

Current in 2.88Ω (3rd diagram):

$$I = \frac{V}{R} = \frac{5.46\text{ V}}{2.88\Omega} = 1.90\text{ A} \quad \rightarrow \text{Series: Same } I$$


Voltage on 1.88Ω (2nd diagram)

$$V = IR = 1.90\text{ A} \cdot 1.88\Omega = 3.56\text{ V} \quad \rightarrow \text{Parallel: Same } V$$

Current in 3Ω (1st diagram)

$$I = \frac{V}{R} = \frac{3.56\text{ V}}{3\Omega} = \boxed{1.19\text{ A}}$$

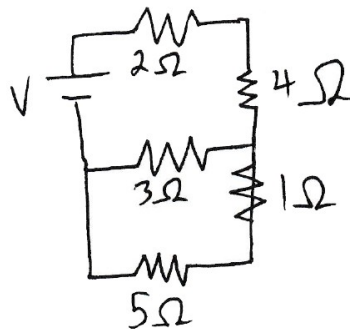Example: If there is 2 V on the 1Ω resistor, what is V , the battery voltage?




On 1Ω : $V = IR$ or $I = \frac{V}{R} = \frac{2\text{ V}}{1\Omega} = 2\text{ A}$

1Ω is in series with 5Ω

$$R_{\text{ser}} = 5\Omega + 1\Omega = 6\Omega$$

Series: Current is the same

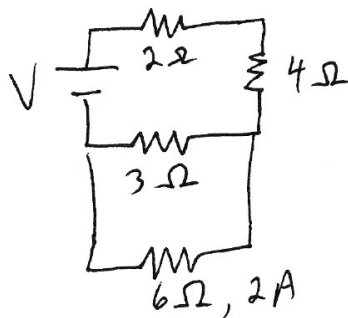


On 6Ω : $V = IR = 2\text{ A} \cdot 6\Omega = 12\text{ V}$

6Ω in parallel with 3Ω

$$\frac{1}{R_{\text{par}}} = \frac{1}{3\Omega} + \frac{1}{6\Omega} = 0.5\Omega^{-1}$$

$$R_{\text{par}} = 2\Omega$$

Parallel: Voltage the same

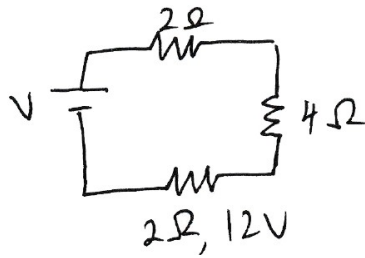


On bottom 2Ω : $I = \frac{V}{R} = \frac{12V}{2\Omega} = 6A$
 Series circuit: same current for all
 $R_{ser} = 2\Omega + 2\Omega + 4\Omega = 8\Omega$
 $V = IR = 6A \cdot 8\Omega = \boxed{48V}$

Section 26-3: Kirchhoff's Rules

- Intersection Rule: Current into junction equals current out

Think about traffic at an intersection

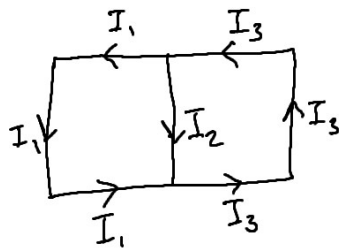When analyzing circuits: currents go from one intersection to the next



$I_1 + I_2 = I_3$ in above diagram

- Loop Rule: $\Delta V = 0$ around a loop

$$\Delta V = - \int \vec{E} \cdot d\vec{\ell} = 0 \text{ (conservative force, like gravity)}$$

- Voltage changes:


V , for batteries

Short end is low voltage



IR , for resistors

High in, low out

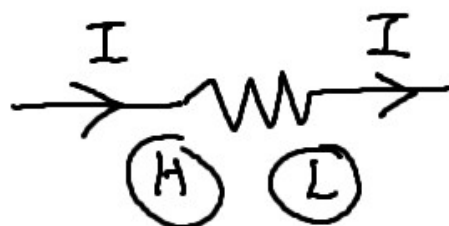

- Steps:

- Label currents, if not given

Currents from one intersection all the way to another


- Do intersection rule

- Label High/Low for each battery/resistor

- Do loop rule

- Starting point / direction do not matter

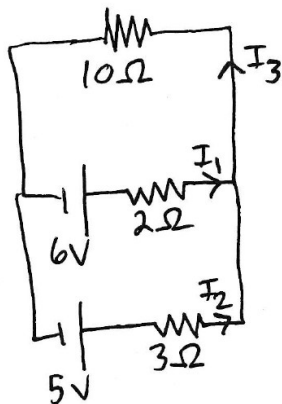Example: Find the voltage drop on $10\ \Omega$ resistor



Left junction: $I_3 = I_1 + I_2$ ①

Right junction: $I_1 + I_2 = I_3$ (redundant)

Top loop: $-10I_3 + 6 - 2I_1 = 0$ ②

Bottom loop: $5 - 3I_2 + 2I_1 - 6 = 0$ ③

Outer loop: $5 - 3I_2 - 10I_3 = 0$ (redundant)

- Must use both rules for every problem!

Some intersections and loops always redundant

- System of equations:

Homework: Use whatever (Wolfram Alpha is free)

Exam: Don't solve for currents, just write down equations

- Above solution is $I_1 = 0.5\text{ A}$, $I_2 = 0$, $I_3 = 0.5\text{ A}$

- If a current is negative: it goes opposite direction to what is drawn

Section 26-5: RC Circuits

- Charging a capacitor


$$V = V_R + V_C$$

$$= IR + \frac{Q}{C}$$

$$= \frac{dQ}{dt} \cdot R + \frac{Q}{C}$$

$$V - \frac{Q}{C} = R \frac{dQ}{dt}$$
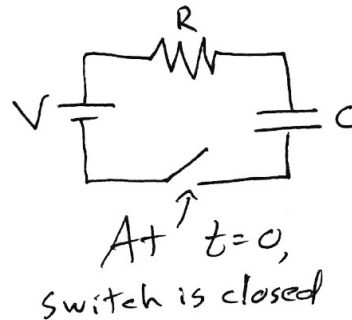
$$dt = \frac{R}{V - Q/C} dQ = \frac{RC}{CV - Q} dQ$$



- Variables are separated, so integrate:

$$\int_0^t dt = \int_0^Q \frac{RC}{CV - Q} dQ$$

$$t = -RC(\ln(CV - Q) - \ln(CV)) = -RC \ln \frac{CV - Q}{CV}$$

$$t = -RC \ln \left(1 - \frac{Q}{CV} \right)$$

$$1 - \frac{Q}{CV} = e^{-t/RC}$$

$$\text{Solve for } Q: \boxed{Q = CV \left(1 - e^{-t/RC} \right)}$$

- How to think of this equation:

$Q = CV$ would be charge if there were no resistor

$1 - e^{-t/RC}$ determines how fast it “turns on”

It is fraction/percent of total of total charge at time t

- Other variables:

$$V_C = \frac{Q}{C} \text{ or } \boxed{V_C = V \left(1 - e^{-t/RC}\right)}$$

$$V_R = V - V_C \text{ or } \boxed{V_R = V e^{-t/RC}}$$

$$I = \frac{V_R}{R} \text{ so } \boxed{I = \frac{V}{R} e^{-t/RC}}$$



- How to think of this equation:

With no capacitor, current is $I = \frac{V}{R}$

As capacitor fills up, current will turn off

$e^{-t/RC}$ is fraction/percent of starting current that remains

- Graphs:

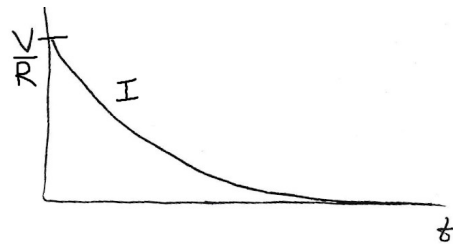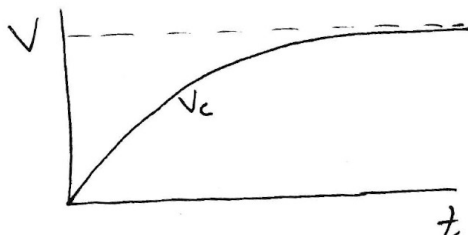

- V_C approaches battery voltage
- I approaches zero (cap. is full, so no more current can flow)
- Also Q approaches full CV
- Full current initially ($I = V/R$)

Example: A $20\mu\text{F}$ capacitor is charged up by a 6V battery through a 12Ω resistor. What is the current when the charge on the capacitor is $30\mu\text{C}$?

$$Q = CV(1 - e^{-t/RC})$$

$$30\mu C = 20\mu F \cdot 6V(1 - e^{-t/RC})$$

Current $30\mu C$ Full charge is $120\mu C$

$$\frac{30\mu C}{120\mu C} = 1 - e^{-t/RC}$$

$$0.25 = 1 - e^{-t/RC}$$

25% charged Current fraction

$$-0.75 = -e^{-t/RC}$$

$$e^{-t/RC} = 0.75$$

$$I = \frac{V}{R} e^{-t/RC}$$

$$= \frac{6V}{12\Omega} \cdot 0.75$$

starting current 75% remains when 25% charged

$$= 0.5A \cdot 0.75 = \boxed{0.375 A}$$

- Discharging a capacitor

$$V_R = V_C$$

Very similar derivation

$$\boxed{Q = CV_0 e^{-t/RC}} \quad V_0 \text{ is initial voltage}$$

$$V_C = \frac{Q}{C} \text{ so } \boxed{V_C = V_0 e^{-t/RC}}$$

$$V_R = V_C \text{ so } \boxed{V_R = V_0 e^{-t/RC}}$$

$$I = \frac{V_R}{R} \text{ so } \boxed{I = \frac{V_0}{R} e^{-t/RC}}$$



At $t=0$, capacitor already charged to V and switch is closed

- Time constant

Because RC determines how fast capacitor is discharged it is called the *time constant* τ (Greek tau), $\tau = RC$

Has units of seconds (exponents must have no units)

Example: A 100 nF capacitor is charged to 20V.

It then discharges through a 15 Ω resistor

After 1.5 time constants, (a) What is the charge on the capacitor? (b) What is the current?

"1.5 time constants" means $t = 1.5 \tau = 1.5 RC$

$$e^{-t/RC} = e^{-1.5RC/RC} = e^{-1.5} = 0.223$$

$$\textcircled{a} \quad Q = CV e^{-t/RC} = 100 \text{ nF} \cdot 20 \text{ V} \cdot 0.223 = \boxed{44.6 \text{ nC}}$$

$$\textcircled{b} \quad I = \frac{V}{R} e^{-t/RC} = \frac{20 \text{ V}}{15 \Omega} \cdot 0.223 = \boxed{0.298 \text{ A}}$$

Homework: Do Chapter 26 in Mastering Physics

Exam #2 on Chapters 24-26

Exam review materials available:

- These lecture notes (Canvas home page)
- Webex recordings (in Canvas under Cisco Webex link)
- Practice exam (Canvas home page)
- Conceptual review practice assignment (in Mastering Physics)
 - Practice for multiple-choice conceptual questions
 - Not for credit but strongly recommended